

**Course Code: EST130****Course Name: BASICS OF ELECTRICAL AND ELECTRONICS ENGINEERING****(2019 Scheme)****PART I: BASIC ELECTRICAL ENGINEERING**

Max. Marks:50

Duration:90min


**PART A***Answer all questions, each carries 4 marks.*

Marks


- |   |  |     |
|---|--|-----|
| 1 | A conductor of length 0.5m kept at right angles to a uniform magnetic field of flux density $2\text{Wb/m}^2$ moves with a velocity of 75 m/s at an angle of $60^\circ$ to the field. Calculate the emf induced in the conductor. | (4) |
| 2 | Define mutual inductance. Two coupled coils of self inductance 0.8H and 0.35H have a coefficient of coupling 0.9. Find the mutual inductance between the coils.  | (4) |
| 3 | State and explain Kirchoff's laws with examples  | (4) |
| 4 | Find the trigonometrical, exponential and polar forms of the vector $8+j6$ .   | (4) |
| 5 | Define (i) active power, (ii) reactive power, (iii) apparent power and (iv) power factor of an ac circuit.   | (4) |

**PART B***Answer one full question from each module, each question carries 10 marks***Module-I**

- |   |  |      |
|---|--|------|
| 6 | Use nodal analysis to find $V_1$ in the given circuit. | (10) |
|---|--|------|

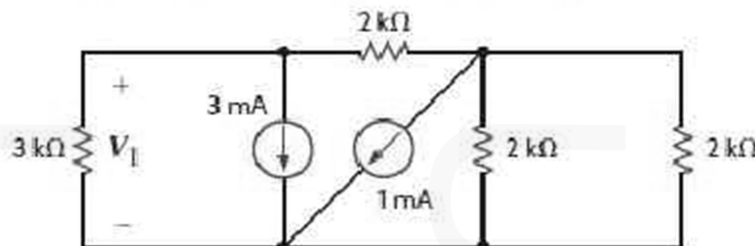**OR**

- |   |   |      |
|---|---|------|
| 7 | Find the current in each branch of the following circuit using mesh analysis? | (10) |
|---|---|------|

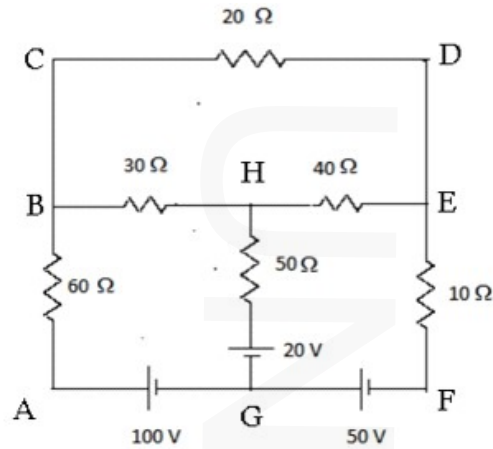


**Module-II**

- 8 An iron ring of cross sectional area  $1\text{cm}^2$  is wound with a coil of 2000 turns. (10)  
 Calculate the magnetising current required to produce a flux of  $0.1\text{ mWb}$  in the iron path if mean length of the path is  $30\text{cm}$  and relative permeability of iron is 2500. Neglect magnetic leakages and fringing.

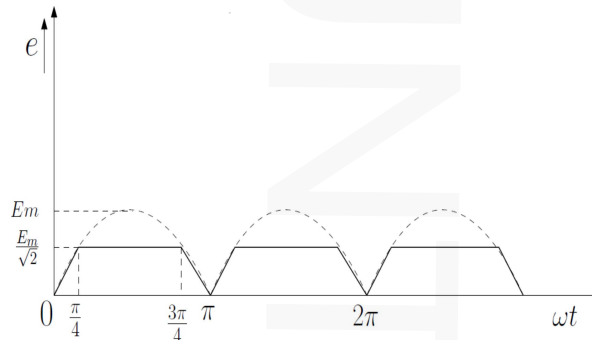**OR**

- 9 A full wave rectified sine function is clipped at  $0.707$  of its maximum value as (10)  
 shown in figure. Find the average and rms values of the function.



**Module-III**

- 10 A sinusoidal voltage  $V=230\angle 15^\circ$  of frequency  $50\text{ Hz}$  is applied to a series RL (10)  
 circuit consisting of  $R=5\ \Omega$  and  $L=0.1\text{ H}$ . Calculate (i) rms current and its phase angle (ii) power factor (iii) average power (iv) reactive power and (v) apparent power drawn by the circuit.

**OR**

- 11 A balanced 3 phase load consists of 3 coils each of resistance  $6\ \Omega$  and inductive (10)  
 reactance of  $8\ \Omega$ . Determine the line current and power absorbed when the coils are (i) star connected (ii) delta connected across  $400\text{V}$ , 3 phase supply.

\*\*\*\*\*

**PART II: BASIC ELECTRONICS ENGINEERING**

Max. Marks: 50

Duration: 90 min

**PART A**

*Answer all questions, each carries 4 marks.*

Marks

- 12 In a 4 band resistor the last colour in the colour band is gold. If the upper range of resistance is  $3.465\Omega$  find its colour code. (4)
- 13 Differentiate between Avalanche breakdown and Zener breakdown? (4)
- 14 Draw and explain the block diagram of a public address system. (4)
- 15 Give reasons for decrease in transistor amplifier gain at low frequencies and high frequencies. (4)
- 16 Explain the relevance of Intermediate Frequency in a superheterodyne receiver. (4)

**PART B**

*Answer one full question from each module, each question carries 10 marks*

**Module-IV**

- 17 a) What are the different types of inductors? Give two typical applications of inductor. (5)
- b) Describe the VI characteristics of PN junction diode. (5)

**OR**

- 18 a) Derive the relation between common base current gain and common emitter current gain, (4)
- b) Sketch the output characteristic of a transistor and explain different regions of operation. (6)

**Module-V**

- 19 a) Explain the working of a full wave bridge rectifier. (5)
- b) Explain the working of an RC coupled amplifier. (5)

**OR**

- 20 a) Describe the working of a zener diode voltage regulator. (5)
- b) Draw and explain the frequency response of an RC coupled amplifier. (5)

**Module-VI**

- 21 a) Draw the frequency spectrum of an amplitude modulated (AM) wave. Given that modulating signal is of frequency  $f_m$  and amplitude  $V_m$  and carrier is of frequency  $f_c$  and amplitude  $V_c$ . Take modulation index as  $m$ . What is the bandwidth requirement of this AM wave? (5)
- b) With a neat sketch explain AM super heterodyne receiver. (5)

**OR**

- 22 a) Describe the principle and block diagram of a GSM system. (5)
- b) Explain the concept of cells and frequency reuse in cellular communication. (5)

\*\*\*\*\*